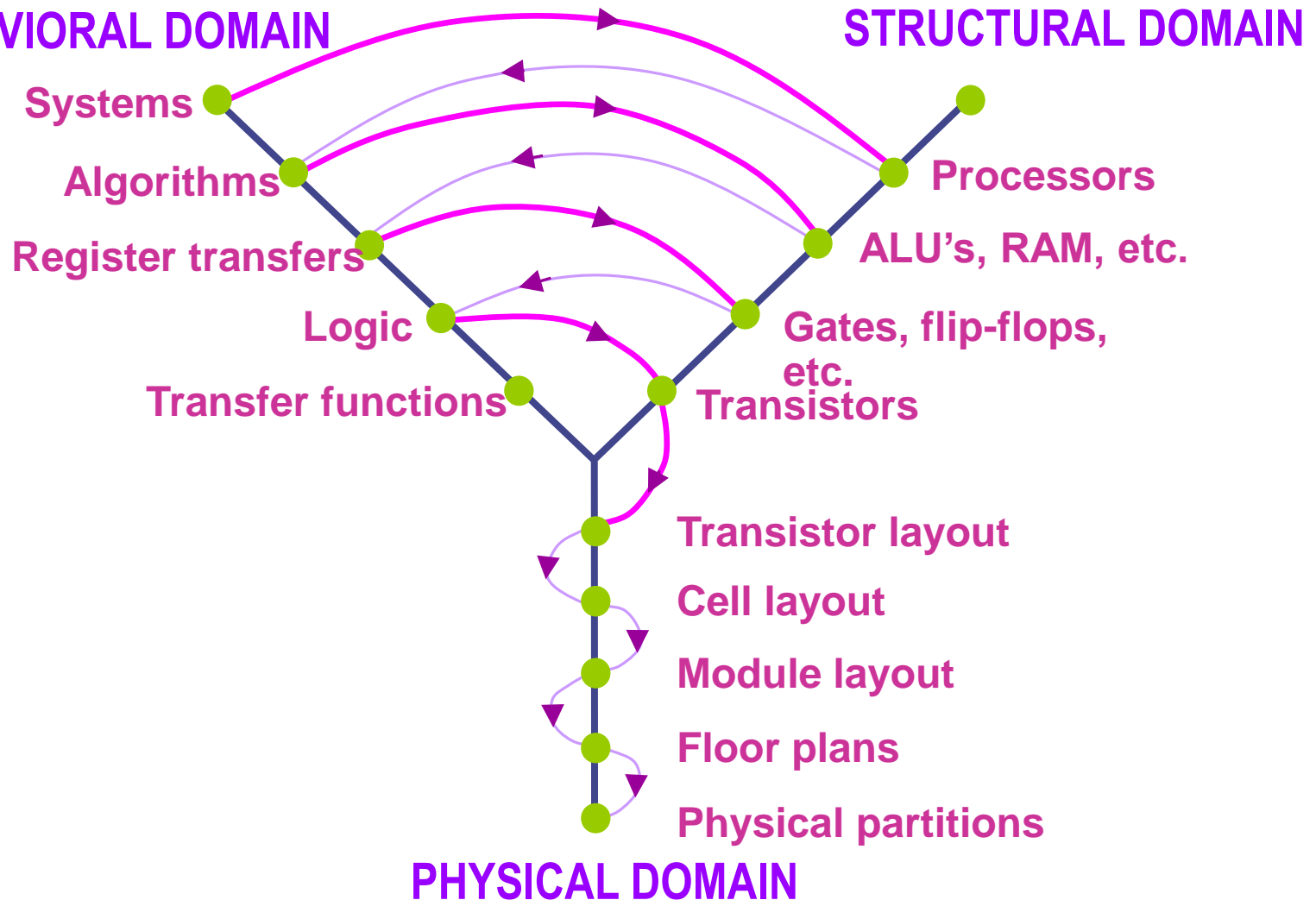





Lab 1: RTL Design of RGB to YUV

Design Flow




Basic Design Flow

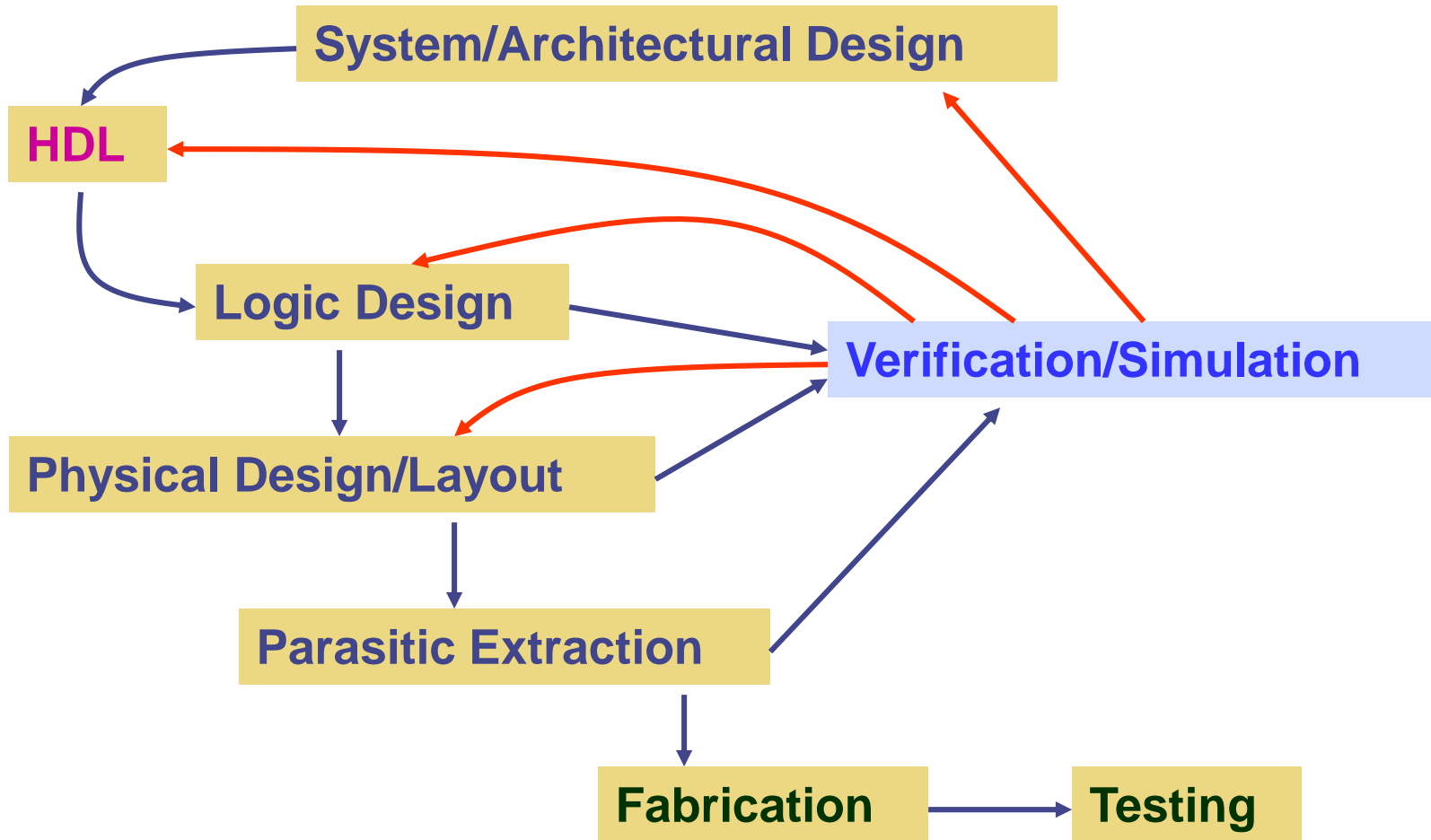

VLSI Design Flow in SoC Era

Traditional ASIC and FPGA Design Flow

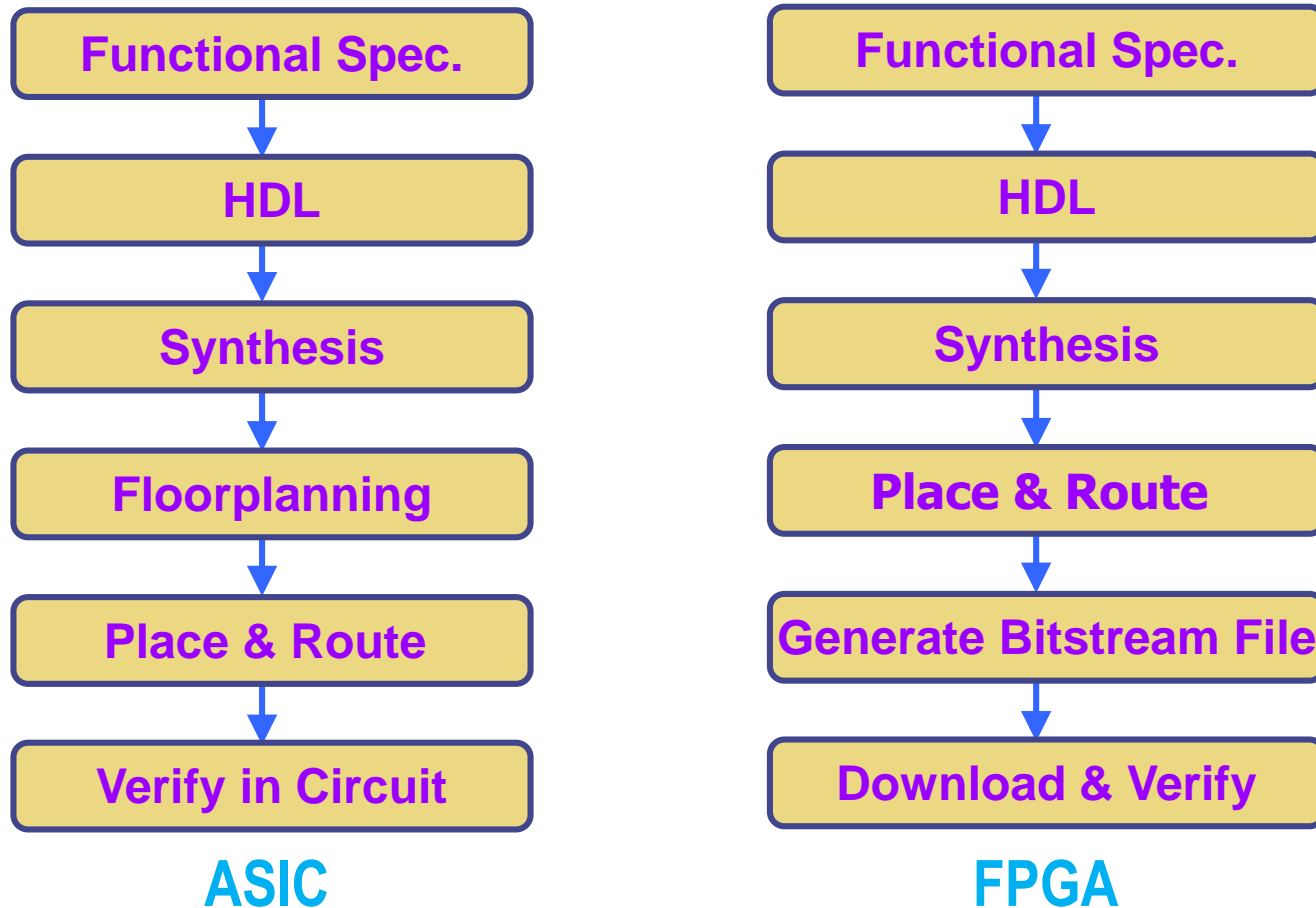

Color Space Conversion

$$\begin{bmatrix} Y \\ C_b \\ C_r \end{bmatrix} = \begin{bmatrix} 0.299000 & 0.587000 & 0.114000 \\ -0.168736 & -0.331264 & 0.500002 \\ 0.500000 & -0.418688 & -0.081312 \end{bmatrix} \begin{bmatrix} R \\ G \\ B \end{bmatrix} + \begin{bmatrix} 0 \\ 128 \\ 128 \end{bmatrix}$$

(a) translate from *RGB* to *YC_bC_r*

$$\begin{bmatrix} R \\ G \\ B \end{bmatrix} = \begin{bmatrix} 1.0 & 0.0 & 1.40210 \\ 1.0 & -0.34414 & -0.71414 \\ 1.0 & 1.77180 & 0.0 \end{bmatrix} \begin{bmatrix} Y \\ C_b - 128 \\ C_r - 128 \end{bmatrix}$$

(b) translate from *YC_bC_r* to *RGB*

RGB to YUV (1/3)



■ Design a RGB to YUV circuit

- ◆ Y : Luminance (明亮度)
- ◆ U and V : Chrominance(色度)

$$Y = 0.299 \times R + 0.587 \times G + 0.114 \times B \quad Y \in [0, 255]$$

$$U = -0.169 \times R - 0.331 \times G + 0.5 \times B + 128 \quad U \in [0, 255]$$

$$V = 0.5 \times R - 0.419 \times G - 0.081 \times B + 128 \quad V \in [0, 255]$$

RGB to YUV (2/3)



**Original
RGB image**



Y (graylevel)



U



V



RGB to YUV (3/3)



$$Y = 0.299 \times R + 0.587 \times G + 0.114 \times B$$

$$U = -0.169 \times R - 0.331 \times G + 0.5 \times B + 128$$




$$V = 0.5 \times R - 0.419 \times G - 0.081 \times B + 128$$

$$Y \in [0, 255]$$

$$U \in [0, 255]$$

$$V \in [0, 255]$$

two's complement

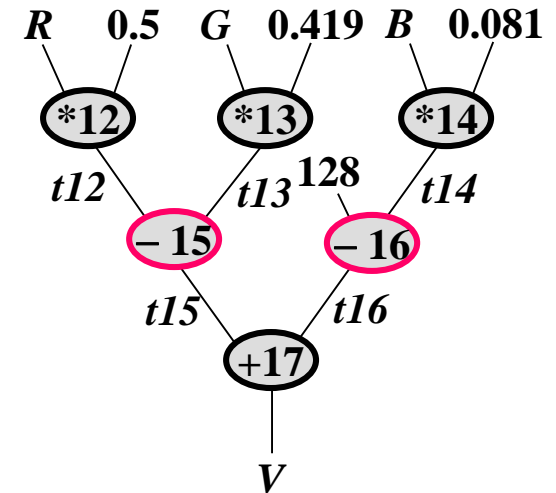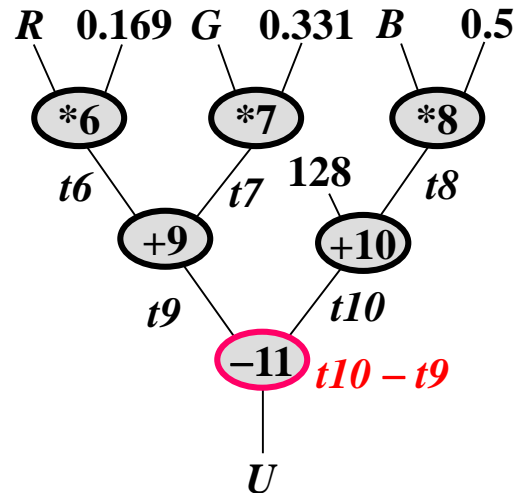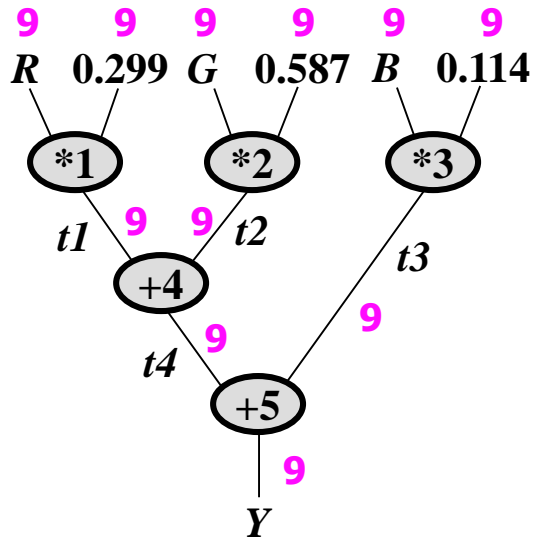

High-level Transformations






$$Y = 0.299 \times R + 0.587 \times G + 0.114 \times B \quad Y \in [0, 255]$$

$$U = \underline{(-0.169)} \times R + \underline{(-0.331)} \times G + 0.5 \times B + 128 \quad U \in [0, 255]$$

$$V = 0.5 \times R + \underline{(-0.419)} \times G + \underline{(-0.081)} \times B + 128 \quad V \in [0, 255]$$


two's complement

  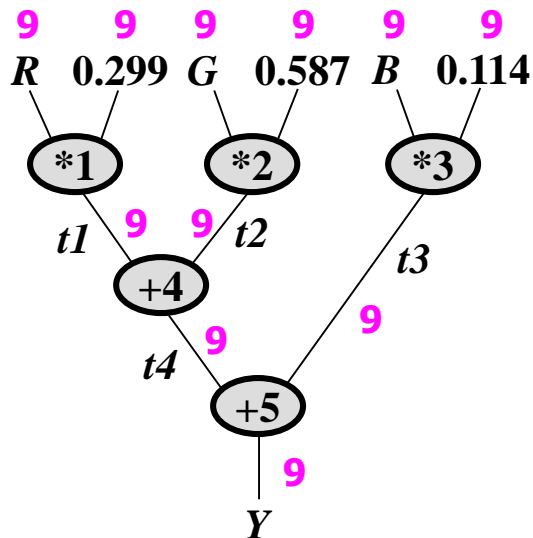


Scheduling of RGB to YUV

Resource constraint:

*	+
1	1

 


Datapath

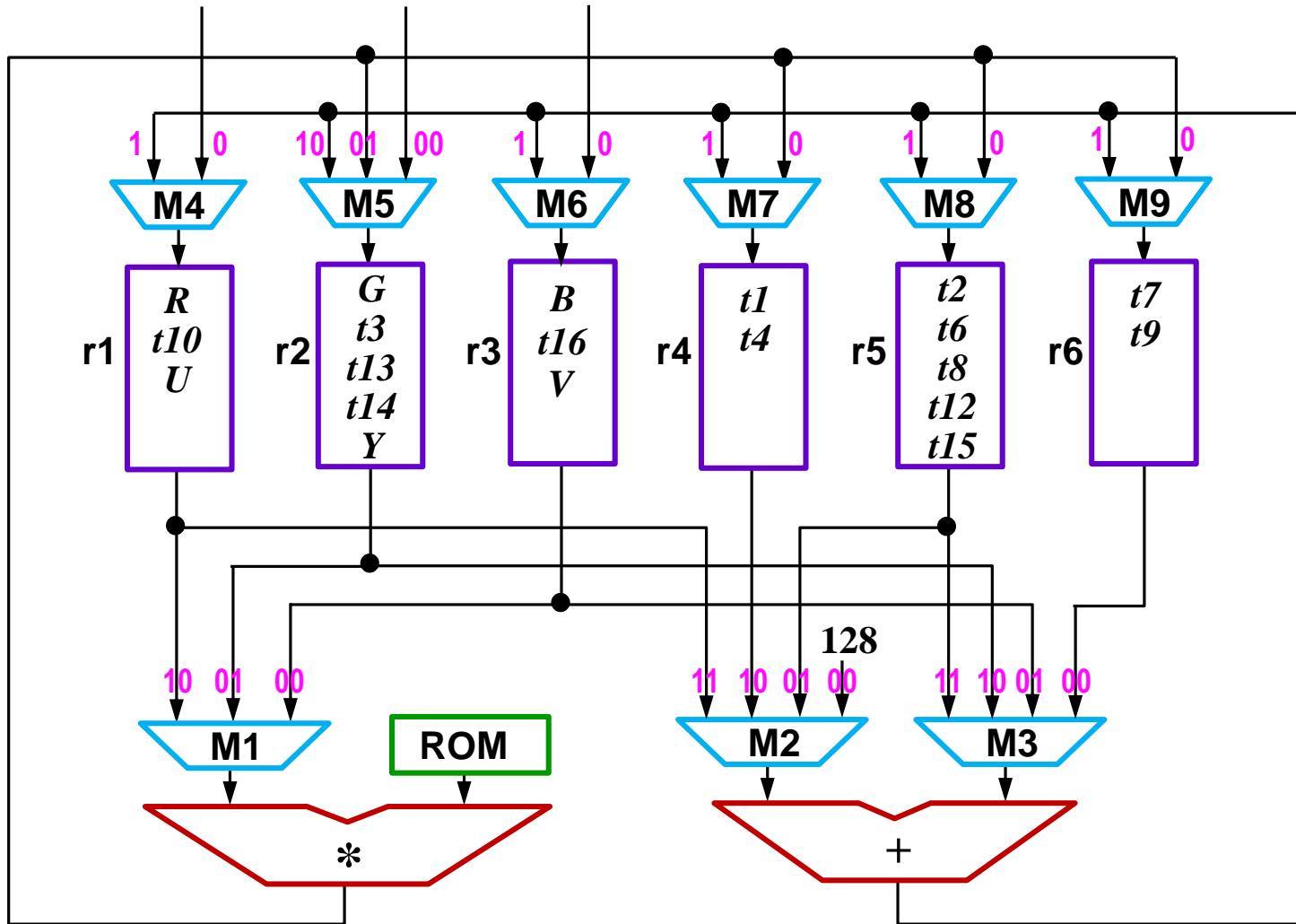

ROM

address	value
000	0.299
001	0.587
010	-0.169
011	-0.331
100	0.5
101	-0.419
110	-0.081
111	0.114

STG and State Table (1/2)

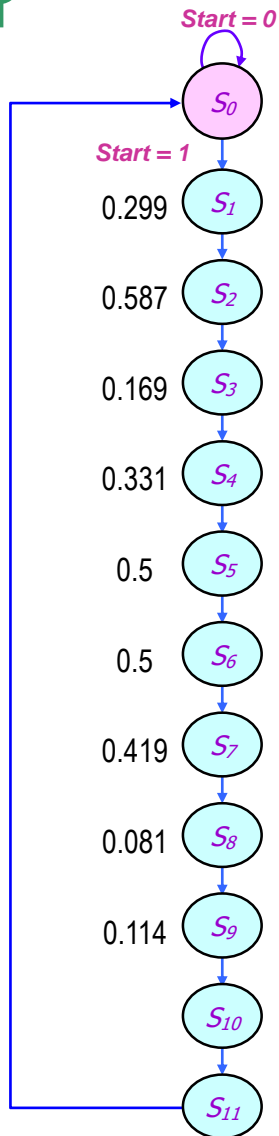

Present State	Input	Next State	Control Signals							
			r1	r2	r3	r4	r5	r6	ROM	done
S0	Start = 0	S0	1	1	1	0	0	0	-	0
	Start = 1	S1								
S1	-	S2	0	0	0	1	0	0	000	0
S2	-	S3	0	0	0	0	1	0	001	0
S3	-	S4	0	0	0	1	1	0	010	0
S4	-	S5	0	0	0	0	0	1	011	0
S5	-	S6	0	0	0	0	1	1	100	0
S6	-	S7	1	0	0	0	1	0	100	0
S7	-	S8	1	1	0	0	0	0	101	0
S8	-	S9	0	1	0	0	1	0	110	0
S9	-	S10	0	1	1	0	0	0	111	0
S10	-	S11	0	1	0	0	0	0	-	0
S11	-	S0	0	0	1	0	0	0	-	1

STG and State Table (2/2)



Present State	Input	Next State	Control Signals								
			M1	M2	M3	M4	M5	M6	M7	M8	M9
S0	Start = 0	S0	-	-	-	0	00	0	-	-	-
	Start = 1	S1									
S1	-	S2	10	-	-	-	-	-	0	-	-
S2	-	S3	01	-	-	-	-	-	-	0	-
S3	-	S4	10	10	11	-	-	-	1	0	-
S4	-	S5	01	-	-	-	-	-	-	-	0
S5	-	S6	00	01	00	-	-	-	-	0	1
S6	-	S7	10	00	11	1	-	-	-	0	-
S7	-	S8	01	11	00	1	01	-	-	-	-
S8	-	S9	00	01	10	-	01	-	-	1	-
S9	-	S10	00	00	10	-	01	1	-	-	-
S10	-	S11	-	10	10	-	10	-	-	-	-
S11	-	S0	-	01	01	-	-	1	-	-	-

Verilog of RGB to YUV (1/8)

Multipliper.v

```
module Mul(A, B, Mul);  
  input signed [`bits-1:0] A, B;  
  output [`bits-1:0] Mul;  
  wire s;  
  wire [7:0] N;
```


```
  assign {s, Mul, N} = A * B;
```

```
endmodule
```

```
module Add(A, B, Add);  
  input signed [`bits-1:0] A, B;  
  output [`bits-1:0] Add;
```

```
  assign Add = A + B;
```

```
endmodule
```

 

Verilog of RGB to YUV (2/8)



`define bits 9 MUX4.v

```
module MUX4 (  
    input  [`bits-1:0] A, B, C, D,  
    input  [1:0] S,  
    output reg [`bits-1:0] Y  
);
```

```
    always @(*) begin  
        case (S)  
            2'b00: Y = A;  
            2'b01: Y = B;  
            2'b10: Y = C;  
            2'b11: Y = D;  
        endcase  
    end
```

endmodule

`define bits 9 MUX3.v

```
module MUX3 (  
    input  [`bits-1:0] A, B, C,  
    input  [1:0] S,  
    output reg [`bits-1:0] Y  
);
```

```
    always @(*) begin  
        case (S)  
            2'b00: Y = A;  
            2'b01: Y = B;  
            2'b10: Y = C;  
            default : Y = A;  
        endcase  
    end
```

endmodule

Verilog of RGB to YUV (3/8)



`define bits 9 Register.v

```
module Register (  
    input  [`bits-1:0] D,  
    input  reset, clk, load,  
    output reg [`bits-1:0] Q  
);
```

```
    always @(posedge clk or negedge reset) begin  
        if(!reset)  
            Q <= 9'b0;  
        else if(load)  
            Q <= D;  
    end
```

```
endmodule
```


Verilog of RGB to YUV (4/8)



```
module ROM (clk, addr, data);    ROM.v
    input    clk;
    input [2:0] addr;
    output reg [8:0] data;

    always @(*)
    begin
        case(addr)
            3'b000: data <= 9'b001001100;
            3'b001: data <= 9'b010010110;
            3'b010: data <= 9'b111010101;
            3'b011: data <= 9'b110101100;
            3'b100: data <= ... ;
            ...
        endcase
    end
endmodule
```

ROM

address	value
000	0.299
001	0.587
010	-0.169
011	-0.331
100	0.5
101	-0.419
110	-0.081
111	0.114

Verilog of RGB to YUV (5/8)



```
`timescale 1ns/1ps  
`define bits 9
```

Datapath.v

```
module Datapath ( inportR, inportG, inportB, control, clk, rst_n, outportY, outportU, outportV, done );  
    input [`bits-1:0] inportR, inportG, inportB;  
    input [21:0] control;  
    input clk, rst_n, done;  
    output [`bits-1:0] outportY, outportU, outportV;  
  
    wire [`bits-1:0] M1_OUT, M2_OUT, M3_OUT, M4_OUT, M5_OUT, M6_OUT, M7_OUT;  
    wire [`bits-1:0] M8_OUT, M9_OUT, Fadd, Fmul, R1, R2, R3, R4, R5, R6, data;  
  
    Register r1( .D(M4_OUT), .reset(rst_n), .clk(clk), .load(control[21:21]), .Q(R1) );  
    Register r2( .D(M5_OUT), .reset(rst_n), .clk(clk), .load(control[20:20]), .Q(R2) );  
    ...  
  
    Register r6( .D(M9_OUT), .reset(rst_n), .clk(clk), .load(control[16:16]), .Q(R6) );  
    MUX3 M1 ( .A(R3), .B(R2), .C(R1), .S(control[12:11]), .Y(M1_OUT) );  
    MUX4 M2 ( .A(9'b01000000), .B(R5), .C(R4), .D(R1), .S(control[10:9]), .Y(M2_OUT) );  
    MUX4 M3 ( .A(R6), .B(R3), .C(R2), .D(R5), .S(control[8:7]), .Y(M3_OUT) );  
    ...  
  
    MUX2 M9 ( .A(Fmul), .B(Fadd), .S(control[0:0]), .Y(M9_OUT) );  
    Mul FU1 ( .A(M1_OUT), .B(data), .Mul(Fmul) );  
    Add FU2 ( .A(M2_OUT), .B(M3_OUT), .Add(Fadd) );  
    ROM FU3 ( .clk(clk), .addr(control[15:13]), .data(data) );  
  
    Register r7(R2, rst_n, clk, done, outportY);  
    Register r9(R1, rst_n, clk, done, outportU);  
    Register r8(R3, rst_n, clk, done, outportV);  
  
endmodule
```

Verilog of RGB to YUV (6/8)



```
`timescale 1ns/1ps
`define bits 9
```

Controller.v

```
`define S0 4'b0000
`define S1 4'b0001
`define S2 4'b0010
`define S3 4'b0011
`define S4 4'b0100
`define S5 4'b0101
`define S6 4'b0110
`define S7 4'b0111
`define S8 4'b1000
`define S9 4'b1001
`define S10 4'b1010
`define S11 4'b1011
```

```
module Controller ( start, rst_n, clk, done, control);
    input start, rst_n, clk;
    output reg done;
    output reg [21:0] control;
```

```
    reg [3:0] Current_State, Next_State;
```

```
    always @(posedge clk or negedge rst_n) begin
        if(!rst_n) Current_State <= `S0;
        else Current_State <= Next_State;
    end
```

```
always @(Current_State or start)
begin
```

```
    case (Current_State)
```

```
        `S0:
```

```
        begin
```

```
            control = 22'b1_1_1_0_0_0_000_00_00_00_0_0_0_0_0_0_0;
```

```
            done = 1'b0;
```

```
            if(~start) Next_State = `S0;
```

```
            else Next_State = `S1;
```

```
        end
```

```
        `S1:
```

```
        begin
```

```
            control = 22'b0_0_0_1_0_0_000_10_00_00_0_0_0_0_0_0_0;
```

```
            done = 1'b0;
```

```
            Next_State = `S2;
```

```
        end
```

```
        ...
```

```
        `S11:
```

```
        begin
```

```
            control = 22'b0_0_1_0_0_0_000_00_01_01_0_00_1_0_0_0_0;
```

```
            done = 1'b1;
```

```
            Next_State = `S0;
```

```
        end
```

```
    default:
```

```
    begin
```

```
        control = 22'b0_0_1_0_0_0_000_00_01_01_0_00_1_0_0_0_0;
```

```
        done = 1'b1;
```

```
        Next_State = `S0;
```

```
    end
```

```
endcase
```

```
end
```

```
endmodule
```

Verilog of RGB to YUV (7/8)



```
`timescale 1ns/1ps    RGB2YUV.v  
`define bits 9
```

```
module RGB2YUV (start, clk, rst_n, inportR, inportG, inportB, done, outportY, outportU, outportV);  
    input  start, clk, rst_n;  
    input  [`bits-1:0] inportR, inportG, inportB;  
    output done;  
    output [`bits-1:0] outportY, outportU, outportV;  
    wire [21:0] control;  
  
    Controller Controller( .start(start), .rst_n(rst_n), .clk(clk), .done(done), .control(control) );  
    Datapath Datapath( .inportR(inportR), .inportG(inportG), .inportB(inportB), .control(control), .clk(clk),  
        .rst_n(rst_n), .outportY(outportY), .outportU(outportU), .outportV(outportV) ,.done(done) );  
  
endmodule
```

Verilog of RGB to YUV (8/8)



```
`timescale 1ns/1ns
`define bits 9
```

testbench.v

```
module testbench();
    parameter half_clk = 20;
    parameter clk_period = 2 * half_clk;
    integer imageIN,imageOUTY,imageOUTU,imageOUTV, i, cc, j;
    integer bmp_width, bmp_height, data_start_index, bmp_size;
    reg [7:0] bmp_data [0:2000000];
    reg rst,clk,start;
    wire [8:0] outY,outU,outV;
    wire done;

    initial begin
        clk = 1'b0;
        rst = 1'b1;
        #(clk_period) rst = ~rst;
        #(clk_period) rst = ~rst;
    end

    always
        #(half_clk) clk = ~clk;

    RGB2YUV rgbtuv(start,clk,rst,...,done,outY,outU,outV);
```

```
    initial begin
        start= 1'b0;
        imageIN = $fopen("mountain256.bmp","rb");
        imageOUTY = $fopen("mountain256Y.bmp","wb");
        imageOUTU = $fopen("mountain256U.bmp","wb");
        imageOUTV = $fopen("mountain256V.bmp","wb");
        cc = $fread(bmp_data,imageIN);
        ...

        for(j = 0; j < 54; j = j + 1) begin
            $fwrite(imageOUTY,"%c",bmp_data[j]);
            $fwrite(imageOUTU,"%c",bmp_data[j]);
            $fwrite(imageOUTV,"%c",bmp_data[j]);
        end

        ...

        #(clk_period*2)
        $fclose(imageOUTY);
        $fclose(imageOUTU);
        $fclose(imageOUTV);
        $fclose(imageIN);
        $stop;

    end


endmodule
```

Scheduling of RGB to YUV



Resource constraint:

*	+
3	3

 


Lab 1: RTL Design of RGB to YUV (1/3)



$$Y = 0.299 \times R + 0.587 \times G + 0.114 \times B$$

$$U = -0.169 \times R - 0.331 \times G + 0.5 \times B + 128$$
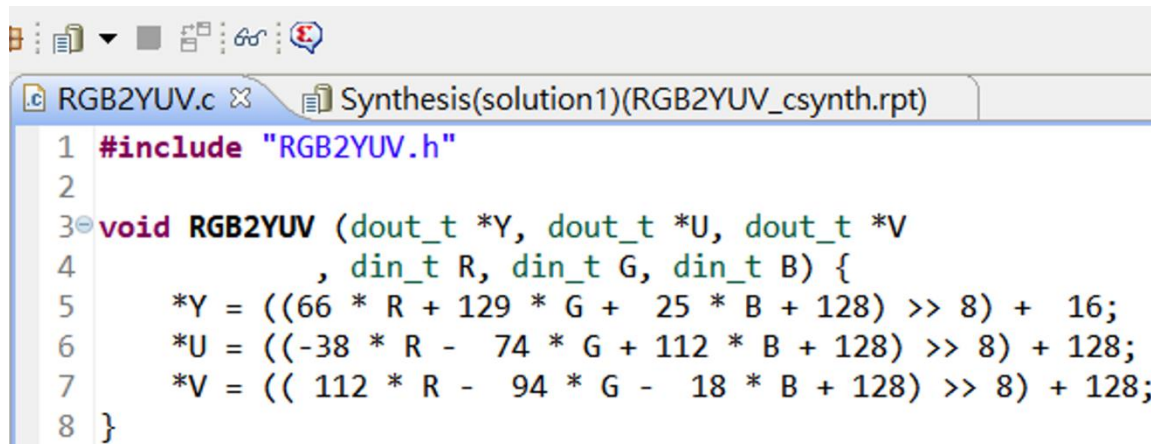
$$V = 0.5 \times R - 0.419 \times G - 0.081 \times B + 128$$



```
1 #include "RGB2YUV.h"
2
3 void RGB2YUV (dout_t *Y, dout_t *U, dout_t *V
4               , din_t R, din_t G, din_t B) {
5     *Y = ((66 * R + 129 * G + 25 * B + 128) >> 8) + 16;
6     *U = ((-38 * R - 74 * G + 112 * B + 128) >> 8) + 128;
7     *V = ((112 * R - 94 * G - 18 * B + 128) >> 8) + 128;
8 }
```

Lab 1: RTL Design of RGB to YUV (2/3)



- Implement the RGB to YUV circuit with **one multiplier and one adder** by using structural (FSM+ Datapath) Verilog code --- Version 1
- Implement the RGB to YUV circuit with **three multipliers, three adders, and initiation interval = 3** by using structural (FSM+ Datapath) Verilog code --- Version 2
- Implement the RGB to YUV circuit with **Vivado HLS** --- Version 3

Lab 1: RTL Design of RGB to YUV (3/3)



- Please list and compare the number of DSPs, LUTs, FFs, clock frequency, and execution cycles of Version 1, Version 2, and Version 3

RGB to YUV	# DSP	# LUT	# FF	Clock Freq.	# Cycle
Version 1					
Version 2					
Version 3					